


ICT 3101

Microwave Engineering


Transmission Line Equations

Transmission Lines of Microwave


Two Parallel Wire Transmission Line

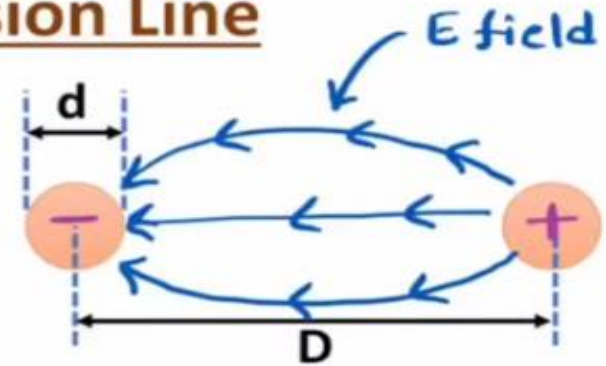



Two Parallel Wire Transmission Line

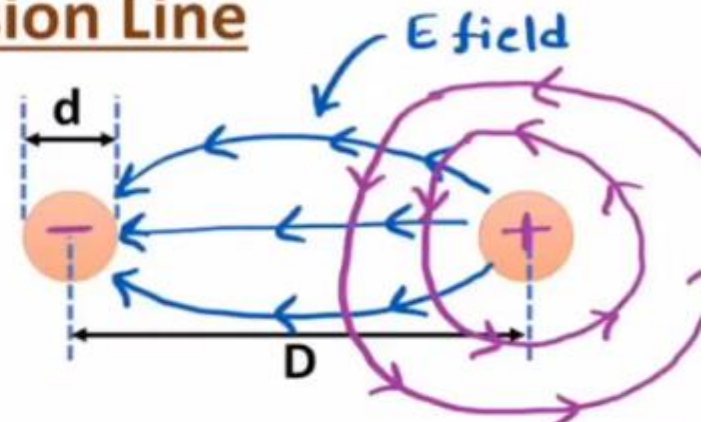

Two Parallel Wire Transmission Line


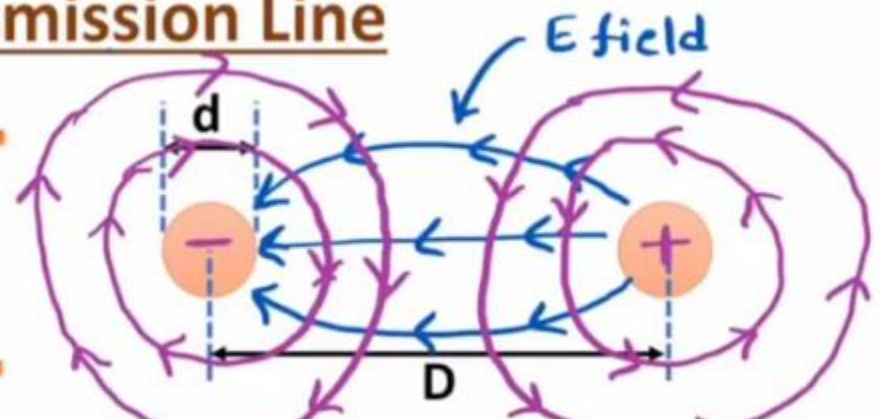


Right Hand Rule

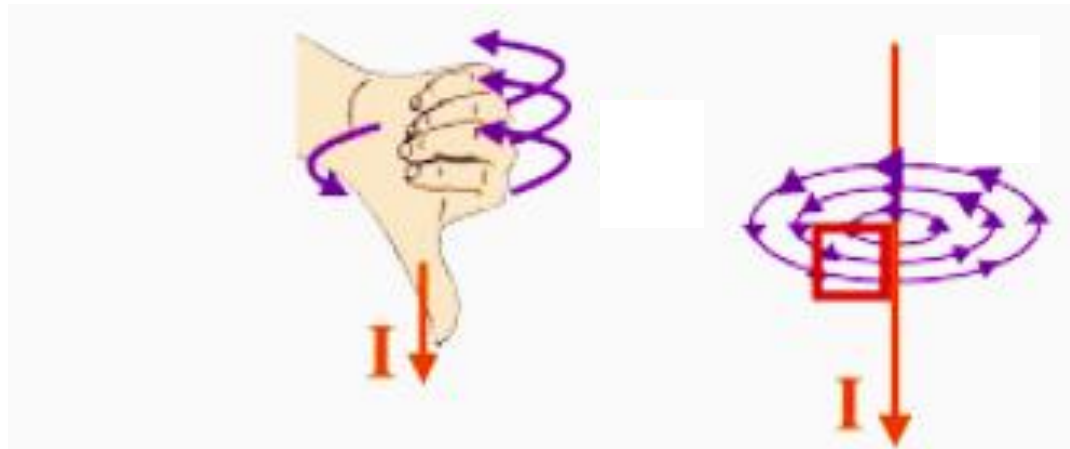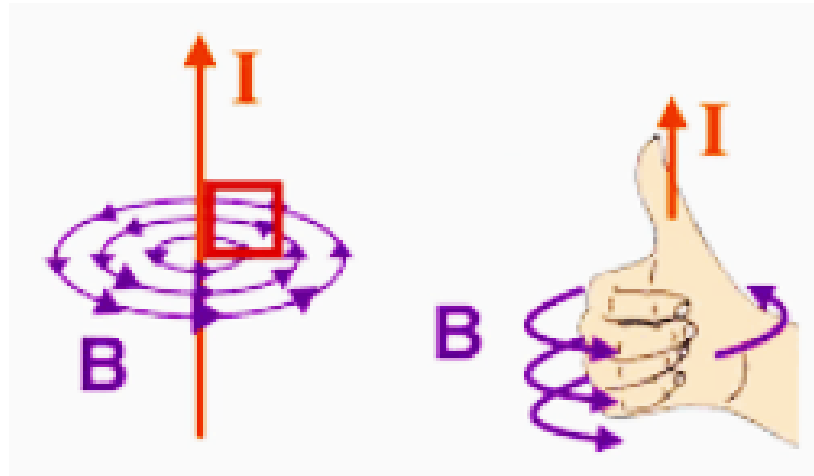


Transmission Line Equations

Two Parallel Wire Transmission Line

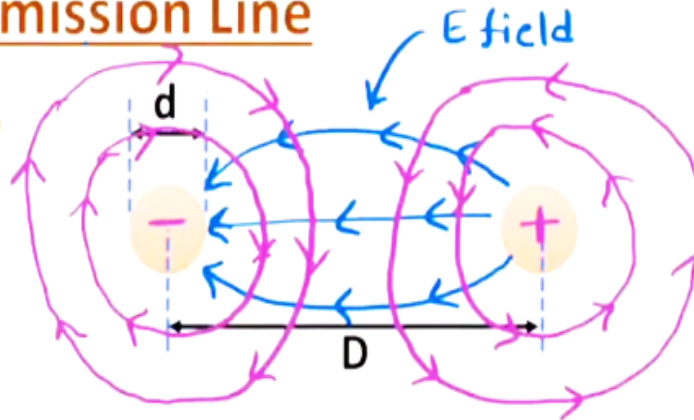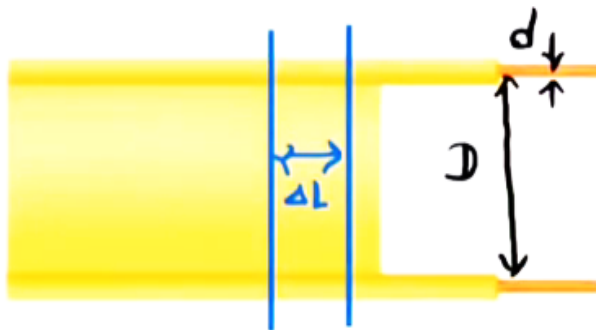

$$L = \frac{\mu}{\pi} \ln \left[\frac{2D}{d} \right]$$
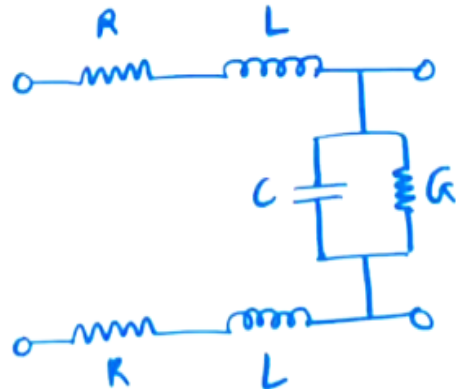
$$C = \frac{\pi \epsilon}{\ln \left[\frac{2D}{d} \right]}$$



→ Characteristics Impedance

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$


→ For Lossless Tx line

$$R = G = 0$$

$$Z_0 = \sqrt{L/C}$$


Transmission Line Equations

Coaxial Transmission Line

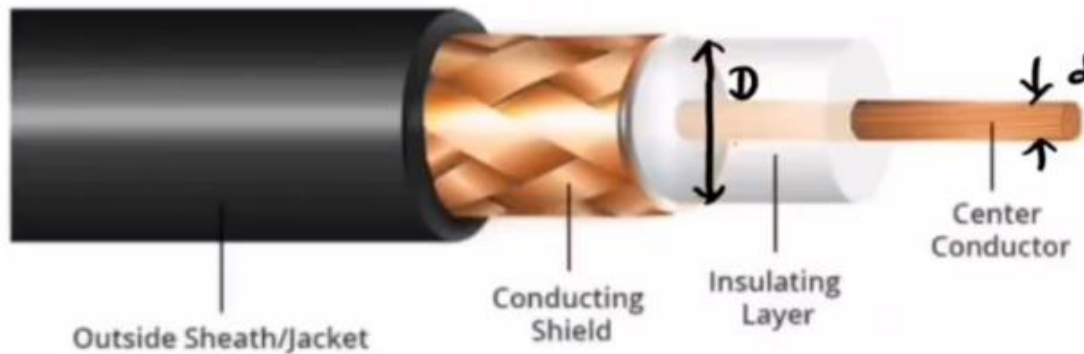


$$L = \frac{\mu}{2\pi} \ln \left[\frac{D}{d} \right]$$
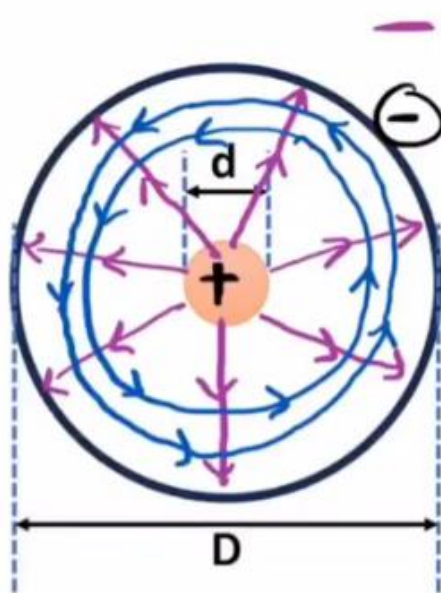
$$C = \frac{2\pi\epsilon}{\ln \left[\frac{D}{d} \right]}$$



$$\rightarrow Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Transmission Line Equations

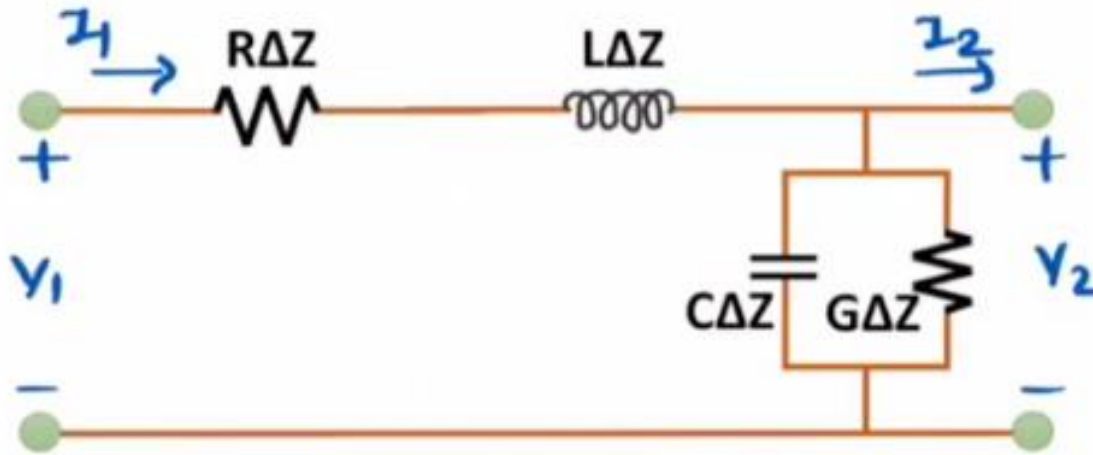

⇒ As per KVL, Voltage drop Across Tx Line

$$\Rightarrow \Delta V = V_2 - V_1 = - \left[R\Delta Z I_1 + L\Delta Z \frac{dI_1}{dt} \right]$$

$$\Rightarrow \frac{\Delta V}{\Delta Z} = - \left[R + L \frac{d}{dt} \right] I_1 \quad \text{--- (1)}$$

⇒ As per KCL, Current drop Across Tx Line

$$\Rightarrow \Delta I = I_2 - I_1 = - \left[G\Delta Z V_2 + C\Delta Z \frac{dV_2}{dt} \right]$$

$$\Rightarrow \frac{\Delta I}{\Delta Z} = - \left[G + C \frac{d}{dt} \right] V_2 \quad \text{--- (2)}$$

Transmission Line Equations

$$\Rightarrow \frac{\Delta V}{\Delta z} = -[R + L \frac{d}{dt}] I_1 \quad \text{--- (1)}$$

$$\Rightarrow \frac{\Delta I}{\Delta z} = -[G + C \frac{d}{dt}] V_2 \quad \text{--- (2)}$$

→ Write eqⁿ (1) & (2) in form of V & I .

$$\Rightarrow \frac{dV}{dz} = -[R + L \frac{d}{dt}] I \quad \text{--- (3)}$$

$$\Rightarrow \frac{dI}{dz} = -[G + C \frac{d}{dt}] V \quad \text{--- (4)}$$

→ Here, $\frac{d}{dt} = j\omega$

$$\Rightarrow \frac{dV}{dz} = -[R + j\omega L] I \quad \text{--- (5)}$$

$$\Rightarrow \frac{dI}{dz} = -[G + j\omega C] V \quad \text{--- (6)}$$

Transmission Line Equations

$$\leadsto \text{Here, } \frac{d}{dt} = j\omega$$

$$\Rightarrow \frac{dV}{dz} = -[R + j\omega L] I \quad \text{--- (5)}$$

$$\Rightarrow \frac{dI}{dz} = -[G + j\omega C] V \quad \text{--- (6)}$$

\leadsto To get Tx line eqⁿ differentiate eqⁿ (5) w.r.t. z

$$\Rightarrow \frac{d^2 V}{dz^2} = -[R + j\omega L] \frac{dI}{dz}$$

$$\Rightarrow \frac{d^2 V}{dz^2} = [R + j\omega L][G + j\omega C] V \quad \text{--- (A)}$$

Transmission Line Equations

~ To get T_x line eqⁿ differentiate eqⁿ (5) w.r.t. z

$$\Rightarrow \frac{d^2 V}{dz^2} = -[R + j\omega L] \frac{dI}{dz}$$

$$\Rightarrow \frac{d^2 V}{dz^2} = [R + j\omega L][G + j\omega C] V \quad \text{--- (A)}$$

~ eqⁿ (A) T_x line eqⁿ and it is similar to wave eqⁿ

$$\Rightarrow \frac{d^2 V}{dz^2} = \gamma^2 V \quad \text{--- (B)}$$

$$\begin{aligned} \gamma &= \text{propagation constant} \\ &= \sqrt{(R + j\omega L)(G + j\omega C)} \end{aligned}$$

~ Solⁿ of eqⁿ (B) is

$$\Rightarrow V = V_1 e^{-\gamma z} + V_2 e^{+\gamma z}$$


Transmission Line Equations

∴ Sol.ⁿ of eq.ⁿ (7) is

$$\Rightarrow V = \underbrace{V_1 e^{-\gamma z}}_{\substack{\uparrow \\ \text{Incident} \\ \text{Signal}}} + \underbrace{V_2 e^{+\gamma z}}_{\substack{\uparrow \\ \text{Reflected} \\ \text{Signal}}}$$

∴ Similarly,
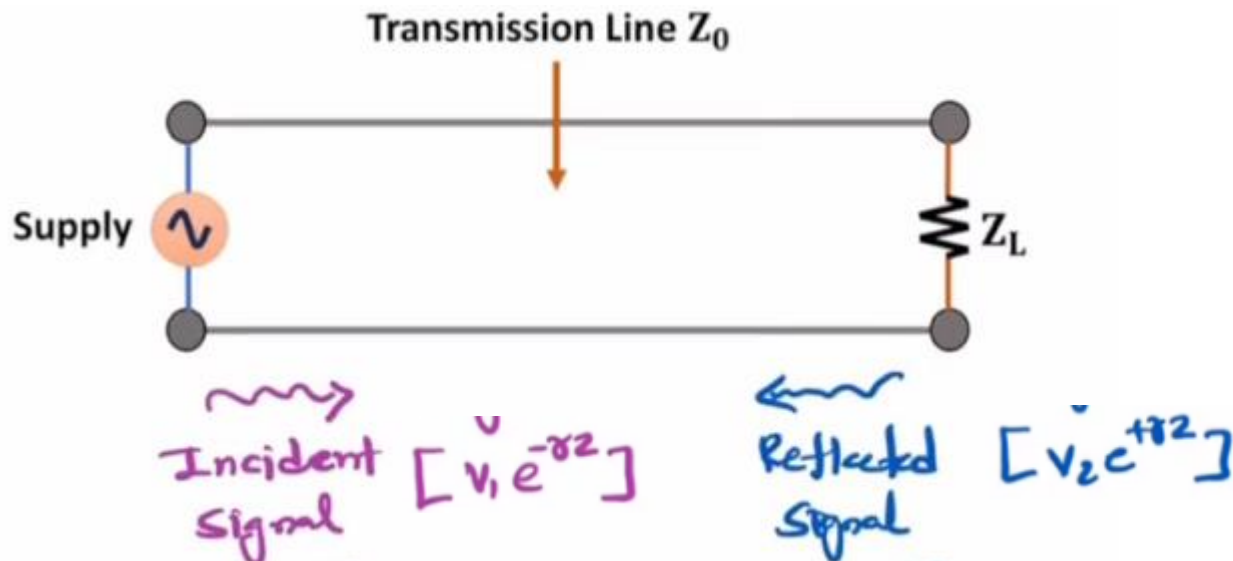
$$\Rightarrow I = \underbrace{I_1 e^{-\gamma z}}_{\substack{\uparrow \\ \text{Incident} \\ \text{Signal}}} + \underbrace{I_2 e^{+\gamma z}}_{\substack{\uparrow \\ \text{Reflected} \\ \text{Signal}}}$$



Propagation Constant, Attenuation Constant and Phase Constant of Transmission Line

→ From Tx line wave eqⁿ

$$\Rightarrow \gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$
$$= \underbrace{\alpha}_{\text{Attenuation Constant}} + j \underbrace{\beta}_{\text{Phase Constant}}$$

→ For lossless Tx line, $[R = G = 0]$

$$\Rightarrow \gamma = \sqrt{(0 + j\omega L)(0 + j\omega C)}$$
$$\Rightarrow \gamma = j\omega\sqrt{LC}$$

$$\Rightarrow \alpha = 0, \quad \beta = \omega\sqrt{LC}$$

→ α and β

$$\Rightarrow \alpha = \frac{1}{2} \left[G\sqrt{\frac{L}{C}} + R\sqrt{\frac{C}{L}} \right]$$

$$\Rightarrow \beta = \omega\sqrt{LC} \left[1 + \frac{1}{8} \left(\frac{R}{\omega L} - \frac{G}{\omega C} \right)^2 \right]$$

Propagation Constant, Attenuation Constant and Phase Constant of Transmission Line

⇒ Sol.ⁿ of wave eq.ⁿ

$$\Rightarrow V = V_1 e^{-\gamma z} + V_2 e^{+\gamma z}$$

⇒ Tx line eq.ⁿ

$$\Rightarrow \frac{dV}{dz} = -(R + j\omega L) I$$

$$\Rightarrow I = \frac{-1}{R + j\omega L} \left(\frac{dV}{dz} \right)$$

$$\Rightarrow I = \frac{-1}{R + j\omega L} \frac{d(V_1 e^{-\gamma z} + V_2 e^{+\gamma z})}{dz}$$

$$\Rightarrow I = \frac{-1}{R + j\omega L} (V_1 (-\gamma) e^{-\gamma z} + V_2 (\gamma) e^{+\gamma z})$$

Characteristics Impedance of Transmission Line

$$\Rightarrow \text{Hence, } \gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\Rightarrow I = \frac{\sqrt{(R + j\omega L)(G + j\omega C)}}{R + j\omega L} (V_1 e^{-\gamma z} - V_2 e^{\gamma z})$$

$$\Rightarrow I = \sqrt{\frac{G + j\omega C}{R + j\omega L}} (V_1 e^{-\gamma z} - V_2 e^{\gamma z})$$

$$\Rightarrow I = \frac{1}{Z_0} (V_1 e^{-\gamma z} - V_2 e^{\gamma z})$$


\Rightarrow Hence, Characteristics Impedance Z_0 is

$$\Rightarrow Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

\Rightarrow For lossless Tx line, $[R = G = 0]$

$$\Rightarrow Z_0 = \sqrt{L/C}$$

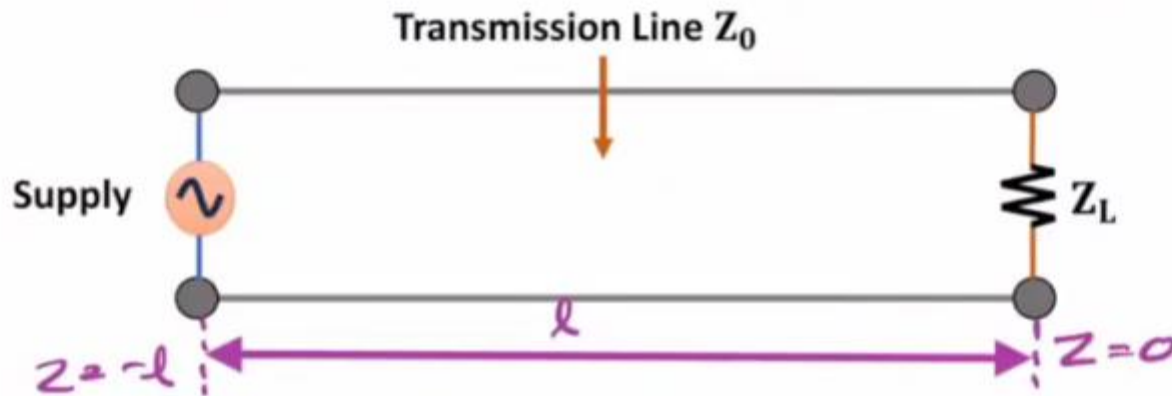Reflection Coefficient of Transmission Line



~> Based on Voltage & Current eq.ⁿ of Tx line

$$\Rightarrow V = \underbrace{V_1 e^{-\gamma z}}_{\text{Incident Signal}} + \underbrace{V_2 e^{\gamma z}}_{\text{Reflected Signal}}$$

$$\Rightarrow I = \underbrace{I_1 e^{-\gamma z}}_{\text{Incident Signal}} + \underbrace{I_2 e^{\gamma z}}_{\text{Reflected Signal}}$$

~> So, above eq.ⁿ are :

$$\Rightarrow V = V_i e^{-\gamma z} + V_r e^{\gamma z}$$

$$\Rightarrow I = I_i e^{-\gamma z} + I_r e^{\gamma z}$$

Reflection Coefficient of Transmission Line

↪ At load $z = 0$

$$\Rightarrow V_L = V_i + V_r$$

$$\Rightarrow I_L = I_i + I_r$$

↪ At source $z = -l$

$$\Rightarrow V_S = V_i e^{\gamma l} + V_r e^{-\gamma l}$$

$$\Rightarrow I_S = I_i e^{\gamma l} + I_r e^{-\gamma l}$$

↪ Characteristic Impedance Z_0

$$\Rightarrow Z_0 = \frac{V_i}{I_i} = -\frac{V_r}{I_r}$$

↪ Reflection Coefficient γ

$$\Rightarrow \gamma = \frac{V_r}{V_i} = -\frac{I_r}{I_i}$$

Reflection Coefficient of Transmission Line



What is VSWR?

Voltage
Standing
Wave
Ratio




What is VSWR?

Voltage
Standing
Wave
Ratio

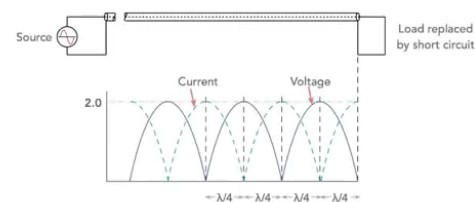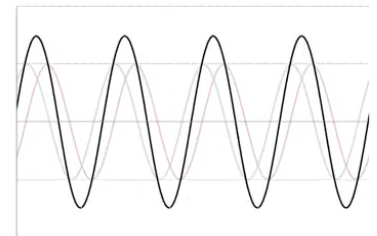


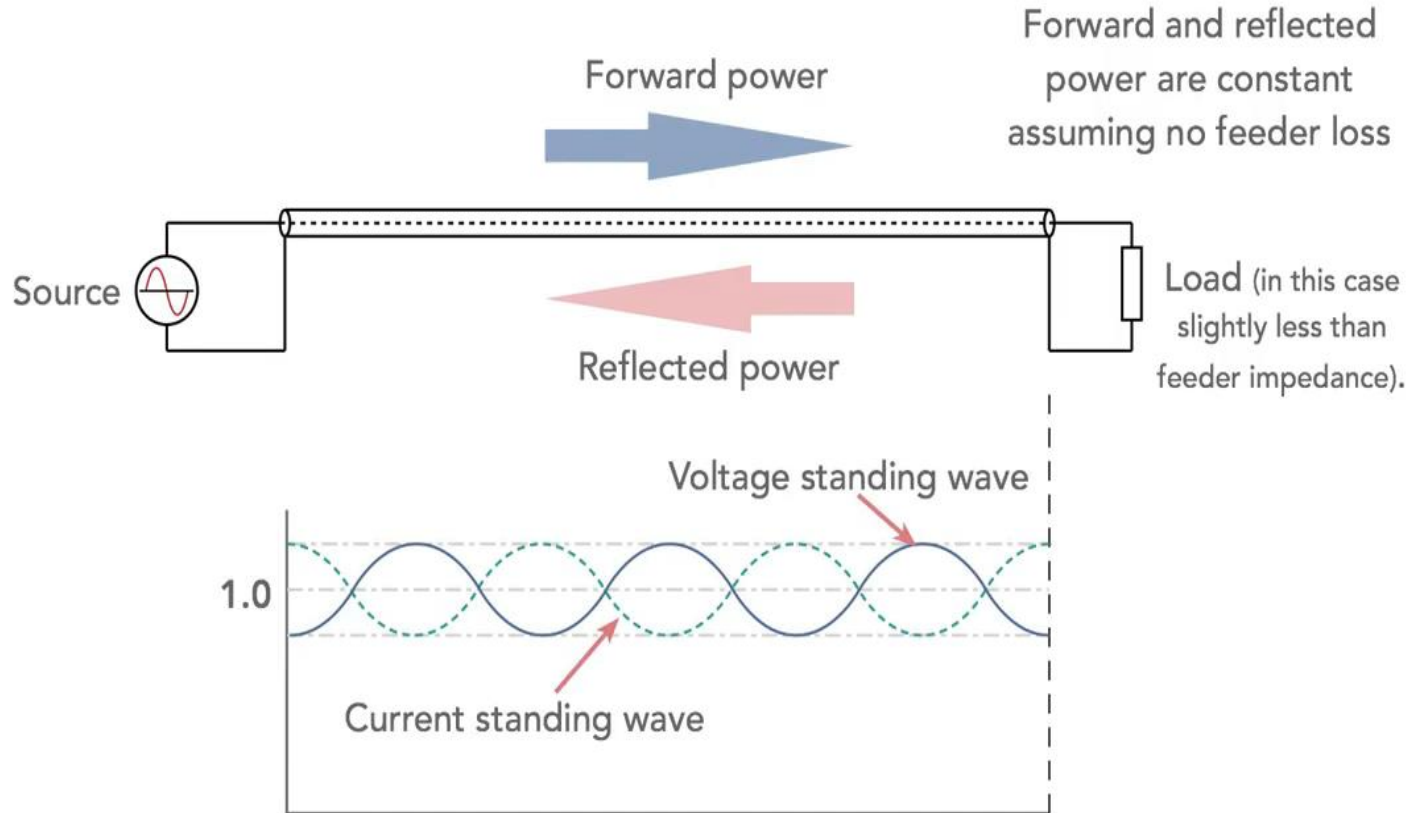Reflection Coefficient of Transmission Line



Reflection Coefficient of Transmission Line

VSWR Definition

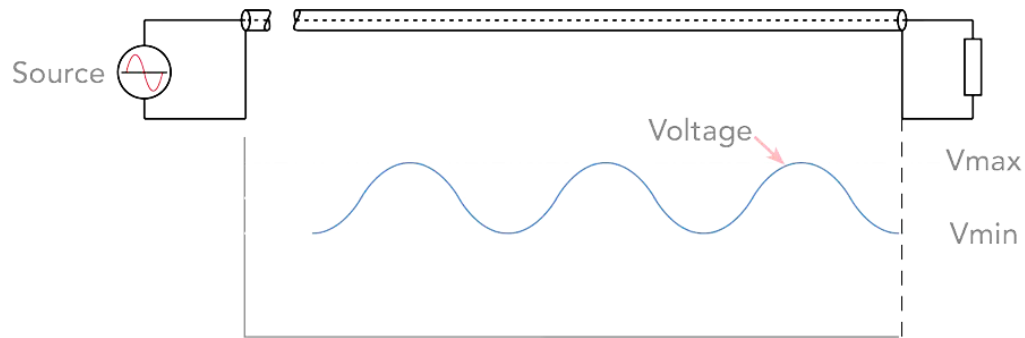

$$VSWR = \frac{V_{max}}{V_{min}}$$

Typical example values

3 : 1 & 2 : 1



Open short circuit = ∞ : 1

Perfect match = 1 : 1

Reflection Coefficient of Transmission Line


What is VSWR?

Voltage
Standing
Wave
Ratio

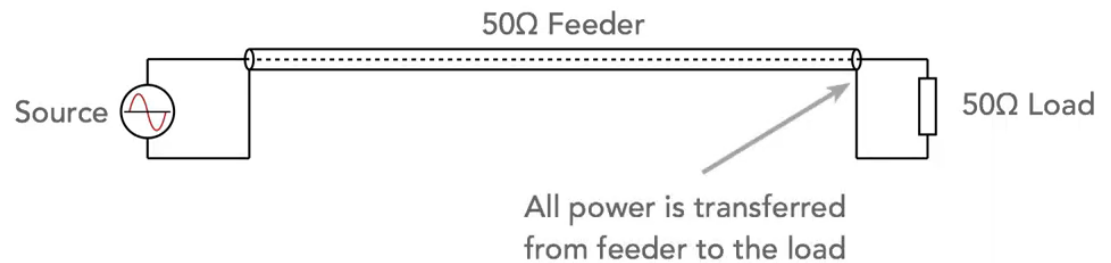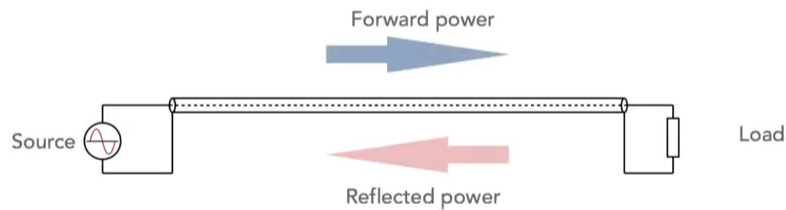

Reflection Coefficient of Transmission Line

Forward & Reverse Power Levels

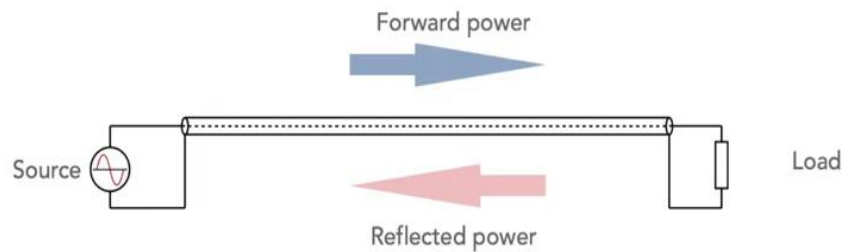

$$VSWR = \frac{1 + \sqrt{P_{ref} / P_{fwd}}}{1 - \sqrt{P_{ref} / P_{fwd}}}$$

Reflection Coefficient of Transmission Line

Summary

- 1) Maximum power is absorbed by a load when load impedance matches the feeder impedance
- 2) When there is a mismatch between feeder and load impedances, power is reflected
- 3) The voltages and currents from the forward and reflected power sum and form standing waves
- 4) It is easy to calculate and also measure VSWR